

**PDFZilla – Unregistered**

**PDFZilla - Unregistered**

**PDFZilla - Unregistered**

Total No. of printed pages = 4

**ET 131304**

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--	--

**2017**

**B.Tech. 3rd Semester End-Term Examination**  
**Computer Science Engineering**  
**DIGITAL SYSTEMS**

Full Marks – 100

Time – Three hours

---

The figures in the margin indicate full marks  
for the questions.

Answer Question No. 1 and any *six* from the rest.

1. Fill in the blanks :

- (a) 9's complement of no 5968 is \_\_\_\_\_.
- (b) In a K map, iff all the cell contains 1, the output becomes \_\_\_\_\_.
- (c) The octal equivalent of  $(10111011)_2$  is \_\_\_\_\_.
- (d) Binary equivalent of  $(1101101)$  grey is \_\_\_\_\_.
- (e) In a X-OR gate, O/P is high only when both the inputs are \_\_\_\_\_.
- (f) Fastest among logic families is \_\_\_\_\_.

**[Turn over**

---

- (g) Race around condition occurs when  $J = \underline{\hspace{2cm}}$  and  $K = \underline{\hspace{2cm}}$ .
- (h) A simple flip-flop is a  $\underline{\hspace{2cm}}$  bit memory.
- (i) In positive logic 5 V is considered as  $\underline{\hspace{2cm}}$ .
- (j) To design a MOD 5 synchronous counter, no of flip flop requires is  $\underline{\hspace{2cm}}$ .
2. (a) Convert the decimal no  $(98)_{10}$  into  $\underline{\hspace{2cm}}$  (5)
- (i) Binary code
- (ii) Grey code
- (iii) BCD code
- (iv) Excess 3 code
- (v) Octal code
- (b) Find the base  $x$   
 $(107)_{10} = (153)_x$  (3)
- (c) Perform the binary addition (2)
- $$\begin{array}{r} 110110 \\ + 110001 \\ + \quad 111 \\ \hline \end{array}$$
- (d) Using 2's complement  $(23)_{10}$  from  $(46)_{10}$ . (5)
3. (a) Realize NAND gate using only NOR gate. (5)
- (b) Prove using Boolean algebra  
 $AB + \bar{A}C = (A + C)(\bar{A} + B)$ . (5)
- (c) Implement the following expression using only NAND gate  $Y = A\bar{B}C + B\bar{C} + \bar{D}$ . (5)

4. (a) Simply using K map  
 $Y = \sum m(0, 1, 2, 3, 5, 7, 10, 13, 15)$ . (5)
- (b) Perform the following BCD addition. (5)
- (i)  $(679.6)_{10} + (536.8)_{10}$
- (ii)  $(342.8)_{10} + (108.9)_{10}$ .
- (c) Expand  $Y = ABC + \bar{B}CD + BD$  to minterm and maxterm. (5)
5. (a) Draw the logic diagram of full adder using two half adder. Justify with logic expression starting from the truth table. (5)
- (b) Design a two bit comparator. (5)
- (c) Design a 8:1 MUX using 4:1 MUX and 2:1 MUX. (5)
6. (a) Explain Race around condition. How it can be avoided? (5)
- (b) Convert SR FF into JK FF. (5)
- (c) What is parity generator? Design an even parity generator. (5)
7. (a) What is counter? Explain different types of triggering. (2)
- (b) Differentiate between asynchronous and synchronous counter with suitable diagram. (3)
- (c) Explain the operation of ring counter with neat diagram. (5)
- (d) What is shift register? What are the modes of operation of a shift register? Explain. (5)

8. (a) Draw the circuit diagram of TTL NAND gate and explain its operation. (8)
- (b) Minimise the following expression using Quine-Mc-Clusky method.  
 $F = \Sigma m(0, 2, 3, 5, 7, 8, 12, 13)$ . (7)
9. (a) Design a MOD 5 synchronous counter using JK flip flop and implement it. (10)
- (b) Write short notes on : (5)
- (i) FPGA
  - (ii) ROM.