

Total No. of printed pages = 4

EC 131701

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

2018

B.Tech. 7th Semester End-Term Examination

LINEAR INTEGRATED CIRCUITS

Full Marks – 100

Time – Three hours

The figures in the margin indicate full marks for the questions.

GROUP A

Answer ALL questions.

1. Choose the correct answer : (10 × 1 = 10)
 - (i) An unity gain amplifier is also known as _____ (difference amplifier/ comparator/ single ended / voltage follower)
 - (ii) If the (+) terminal of an inverting op-amp is connected to the ground the (-) terminal will _____ (not need an input resistor/ be virtual ground / have high reverse current / not invert the signal)
 - (iii) Differential gain and common-mode gain ratio is called as _____ (Amplitude / Differential – mode rejection / Common mode rejection / Phase)

[Turn over