

7. (a) Draw the internal structure of the Cathode Ray Tube. List and explain the main parts of the CRT. (10)
- (b) Draw circuit diagram and equation for output voltage when an op-amp is used as:
- (i) Inverter,
- (ii) Adder. (5)
8. (a) Draw the block diagram of a Dual Slope Integrating A/D Converter and explain how it works. (10)
- (b) Differentiate between Digital and Analog instruments. (5)
9. Write short notes (any three): (3×5=15)
- (a) Digital Multimeter
- (b) Q- meters
- (c) Frequency Meter
- (d) Binary Weighted Resistance D/A Converter.

Total No. of printed pages = 4

EC 131305 OR

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

2019

B.Tech. (ECE) 3rd Semester End-Term Examination

**ELECTRONIC MEASUREMENT AND INSTRUMENTATION**

(Old Regulation)

Full Marks = 100

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer question No. 1 and any six from the rest.

1. Answer the following : (MCQ/Fill in the blanks) (10 × 1 = 10)
- (i) \_\_\_\_\_ instruments are used for direct current measurements only.
- (ii) The unit of Energy is \_\_\_\_\_.
- (iii) Two bridges used for measuring resistance are \_\_\_\_\_ and \_\_\_\_\_.
- (iv) Voltmeters are always connected in \_\_\_\_\_ in a circuit.
- (v) \_\_\_\_\_ instruments are the cheapest disregarding the accuracy.

[Turn over

- (vi) The conditions for balance of an AC bridge are \_\_\_\_\_ and \_\_\_\_\_.
- (vii) The temperature error in ammeters can be eliminated by using a \_\_\_\_\_.
- (viii) Output impedance of an ideal op-amp is \_\_\_\_\_.
- (ix) The torques required for satisfactory operation of an indicating instrument are \_\_\_\_\_ and \_\_\_\_\_.
- (x) Flash Converters are used for \_\_\_\_\_ conversion.
2. (a) Explain the construction of D' Arsonval Galvanometer with proper labeled diagram. (6)
- (b) What is an ohmmeter? Draw circuit diagram for a shunt type ohmmeter. (3)
- (c) Mention a few advantages and disadvantages of PMMC Instruments. (6)
3. (a) A moving coil instrument gives a full scale deflection of 10mA when the potential difference across the terminals is 100mV. Calculate:
- (i) The shunt resistance for a full scale deflection corresponding to 100 A
- (ii) The series resistance for full scale reading with 1000 V.
- Calculate the power dissipation in each case. (7)
- (b) Briefly explain what is coupling torque. (3)

- (e) For a certain dynamometer ammeter the mutual inductance  $M$  varies with deflection  $\theta$  (expressed in degrees) as :
- $$M = -6 \cos(\theta + 30^\circ) \text{ mH.}$$

Find the deflecting torque produced by a direct current of 50 mA corresponding to a deflection of  $60^\circ$ . (5)

4. Explain with circuit diagram (derive the balanced condition): (7.5×2=15)
- (a) Maxwell Bridge
- (b) Schering Bridge.
5. (a) Design a multi-range d.c. milli-ammeter using a basic movement with an internal resistance  $R_m = 50 \Omega$  and a full scale deflection current  $I_m = 1 \text{ mA}$ . The ranges required are 0-10 mA, 0-50 mA, 0-100 mA and 0-500 mA. (6)
- (b) List some errors encountered in electro-dynamometer type instruments. (4)
- (c) What is the resolution of a  $3\frac{1}{2}$  digits display? Also find the resolution of a  $3\frac{1}{2}$  digit meter in case its range is 1 V. (5)
6. (a) Draw a commonly used sample- hold circuit and explain the operation of Sample-Hold Circuits. (7)
- (b) What is the use of digital electronic counters? With proper figure explain a decade counter. (2+6)