

Total No. of printed pages = 6

**ET 131305 OR**

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

**2019**

**B.Tech. (EE) 3<sup>rd</sup> Semester End-Term Examination**

**ANALOG ELECTRONICS**

**(Old Regulations)**

Full Marks – 100

Time – Three hours

---

The figures in the margin indicate full marks  
for the questions.

(Answer to Question no.1 and any *six* from the rest.)

1. Answer *all* questions :

(10 × 1 = 10)

- (i) What do you mean by donor acceptor impurities?
- (ii) What is the energy band gap of Ge at 300K?
- (iii) Define mass – action law.
- (iv) Define dynamic resistance of a diode.
- (v) What is a transistor? Why is it so called?
- (vi) Why is collector wider than emitter and base?
- (vii) What do you mean by feedback in amplifiers?

[Turn over

(viii) For an inverting amplifier, if  $R_1 = 1k\Omega$  and  $R_f = 10 k\Omega$ . The closed loop gain is

- (a) 10                      (b) 11  
(c) -10                     (d) 100

(ix) Define CMRR in op-amps.

(x) If transistor has a  $\alpha = 0.97$ , the value of  $\beta$  is

- (a) 0.03                    (b) 32.33  
(c) 200                     (d) 100

2. (a) What do you mean by Fermi level? Draw Fermi energy level for p-type, n-type and intrinsic semiconductor. (5+10=15)

(b) Define mean free path and mean free time.

Find the conductivity of silicon:

- (i) in intrinsic condition at 300K  
(ii) with donor impurity of 1 in  $10^8$   
(iii) with acceptor impurity of 1 in  $5 \times 10^7$   
(iv) with both the above impurities simultaneously

Given that for silicon at room temperature  $n_i = 1.5 \times 10^{10}/\text{cm}^3$ ,  $\mu_n = 1300 \text{cm}^2/\text{V-s}$ ,  $\mu_p = 500 \text{cm}^2/\text{V-s}$  and number of silicon atoms/ $\text{cm}^3 = 5 \times 10^{22}$ .


3. (a) Describe P-N junction in forward bias and reverse bias conditions. (5+10=15)

(b) Explain the formation of the depletion region in P-N junction diode with the derivation of the depletion width.

(a) Determine the forward resistance of a P-N junction diode when the forward current is 5mA at  $T=300\text{K}$ . Assume silicon diode. (5+5+5=15)

(b) Draw the comparison of CB, CC, CE configuration of BJT.

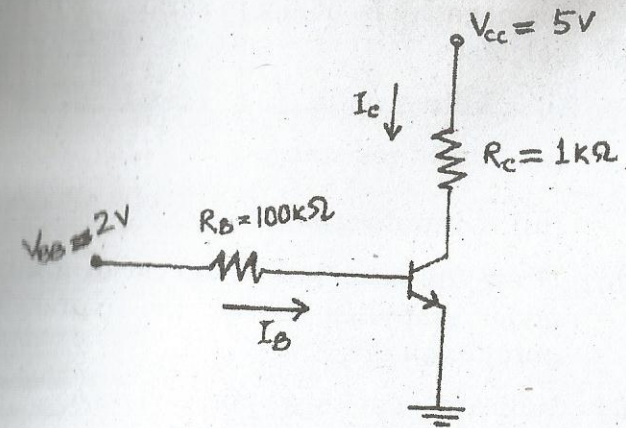(c) Determine the base, collector and emitter currents and  $V_{CE}$  for a CE circuit shown below. For  $V_{CC}=5\text{V}$ ,  $V_{BB}=2\text{V}$ ,  $R_B=100k\Omega$ ,  $R_C=1k\Omega$ ,  $V_{BE}=0.7\text{V}$ ,  $\beta=100$ .



5. (a) Describe the Ebers-Moll model with circuit diagram.

(b) Describe the operation of NPN transistor in CB configuration.

(c) Find  $I_B$ ,  $I_C$ ,  $V_{CE}$  and  $S$  for fixed bias circuit. Given,  $V_{CC}=16\text{V}$ ,  $R_B=470k\Omega$ ,  $R_C=2.7k\Omega$ ,  $\beta=90$  (5+5+5=15)

6. (a) What is early effect? Define punch through. (4+4+3+4=15)
- (b) Why the stability of Q-point is necessary? What are the causes of instability of a Q-point?
- (c) Explain how negative feedback amplifier helps in reducing distortion and noise?
- (d) What are the different ways of connecting a feedback signal in an amplifier? Derive an expression for input resistance of a voltage series feedback.

7. (a) An amplifier with  $2.5K\Omega$  input resistance and  $50K\Omega$  output resistance has a voltage gain of 100. The amplifier is now modified to provide 5% negative feedback in series with the input, calculate

- (i) Voltage gain  
 (ii) Input resistance  
 (iii) Output resistance (5+5+5=15)

- (b) Draw the schematic diagram of a summing adder amplifier. Derive the expression of the output voltage.


- (c) Indicate a op-amp connected as a

- (i) Scale changer  
 (ii) High pass filter  
 (iii) Subtractor  
 (iv) Voltage follower  
 (v) Integrator


For each case get the relevant expression for  $V_{out}$ .

- (a) Draw the pin configuration of IC 741. Define input offset voltage, input bias current and input offset current. (5+5+5=15)

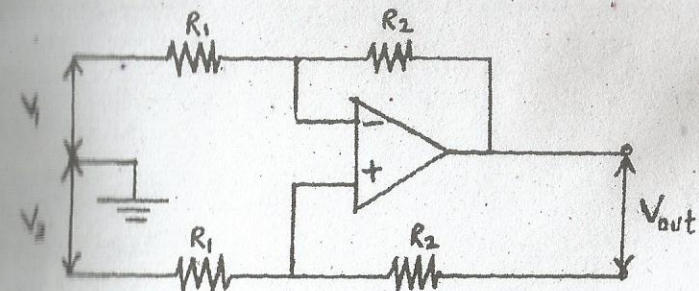- (b) Prove that  $V_{out} = \frac{R_2}{R_1}(V_2 - V_1)$  for the circuit shown.



- (c) Find the output voltage  $V_{out}$

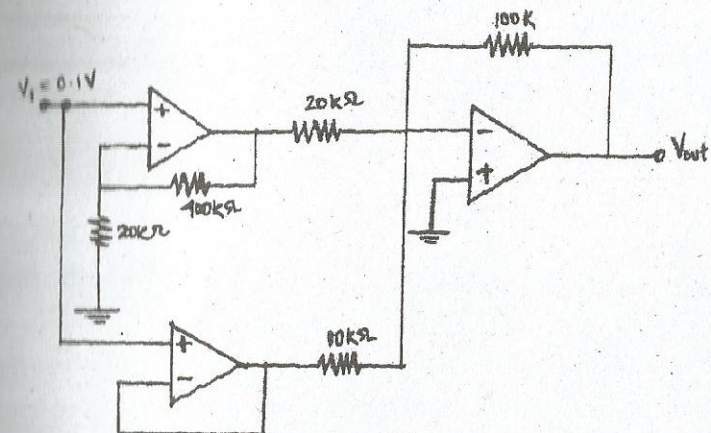

9. Write short notes on (any three)

(5+5+5=15)

- (a) Avalanche breakdown
- (b) Topologies of feedback amplifiers
- (c) Voltage divider biasing
- (d) Operating modes of op-amp