

Roll No:

--	--	--	--	--	--	--	--	--	--

The Assam Royal Global University, Guwahati

Royal School of Information Technology
BCA/B.Sc.IT 1st Semester

Semester End Examination, January 2023
Course Title : Digital Logic & Computer Design
Course Code : CAP052C103/INT052C103

Time: 3 Hours

Maximum Marks: 70

Note: Attempt all questions as per instructions given.
The figures in the right-hand margin indicate marks.

Section – A

1. Attempt all questions.

2 x 8

- Define radix.
- How is a digital system different from an analog system?
- Define associative law in Boolean Algebra.
- Define a logic gate.
- What is a multiplexer?
- What is an adder circuit?
- What is edge triggering?
- Define EPROM.

Section – B

2. Attempt any two of the following:

6 x 2

- Convert the numbers into desired base. (i) $(A6BF5)_{16} = ()_2$, (ii) $(101.01)_2 = ()_{10}$, (iii) $(7.FD6)_{16} = ()_8$, (iv) $(345)_8 = ()_{10}$, (v) $(7864)_{10} = ()_{16}$
- Write the truth table and logic symbol of EX-OR and EX-NOR Gate. Implement the following expression in logic circuit: $ABC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C}$
- Write a note on BCD codes. Convert the Gray code 111011 to binary form.

3. Attempt any two of the following:

7 x 2

- What is a Karnaugh map? Using the K-map method, simplify the following function and obtain the minimal sum of product expression: $f(w,x,y,z) = \sum(1,3,4,5,6,7,9,12,13)$. Also implement the simplified expression using basic logic gates.
- Explain the terms with examples: (a) Prime Implicants, (b) Input Variable, (c) Minterm and (d) Maxterm.
- Using the Quine McCluskey method, obtain the minimal sum of product expression of the following function: $Y = \sum(0,2,3,6,7,8,10,11,12,15)$

4. Attempt any two of the following:

7 x 2

- Explain, in details, full adder circuit, with truth table and derivation of logic expression.
- What is an encoder? Derive the logic expression and logic diagram for a octal-to-binary encoder.
- Write a note on EPROM & EEPROM.

5. Attempt any one of the following:

14 x 1

- How is a flip-flop different from a latch? Explain in details, the Master Slave flip flop.
- What is a counter? Mention few applications of Counters. Explain in details, the Ring Counter.