



Total No. of printed pages = 2

SUBJECT CODE = INT052104

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

2017

End Semester B.Sc. (IT) Examination

1st Semester

INTRODUCTION TO DIGITAL LOGIC

Full Marks- 70

Pass Marks- 21

Time- 3 hours

The figures in the margin indicate full marks.

PART – A

Q.1. Answer all questions:

(16x1=16)

- Convert $(1100101011.1110)_2$ to hexadecimal equivalent.
- Convert $(3000.45)_{10}$ into its equivalent octal number.
- Which gates are called as Universal Gates?
- Find the dual of following Boolean expression: $(A+B)(A+C)=A+BC$
- What is a full adder?
- What is a parity bit generator?
- What is a demultiplexer?
- What is a decoder?
- Draw the logic diagram for a gated S-R Latch
- What is a flip-flop?
- What are the two basic types of counters?
- Give some applications of shift registers.
- Name the three types of TTL gates.
- Which is the fastest and the slowest logic family?
- Give the classification of logic families.
- What is propagation delay?

PART – B

Q.2. Answer all questions:

(4x3.5=14)

- What is Duality theorem? Reduce the expression: $f=A[B+\overline{C}]\overline{((AB+AC))}$
- Give the comparison between combinational and sequential circuits.
- Using K-map, simplify the following function: $F(a,b,c,d)=\sum(1,4,6,7,8,9,10,11,15)$
- Explain the function of 3-input TTL NAND gate.

PART – C

Q.3. State and prove De-Morgan's Theorem.

(10)

OR

Minimize the following logic function using Quine-Mc-Cluskey method:
 $(A,B,C,D)=\sum m(0,1,2,3,5,7,8,9,11,14)$

(10)

Q.4. Explain the look ahead carry generators and discuss its utility in adders.

(10)

OR

Implement a full adder circuit using two half adders.

(10)

Q.5. Explain the working of a master-slave JK flip flop. Explain how it overcomes race-around condition.

(10)

OR

Explain the operation of Serial-in-Serial-out shift register.

(10)

Q.6. Explain the working of NAND gate using n-channel MOS logic circuit.

(10)

OR

With the help of logic diagram and circuit diagram explain static RAM cell.

(10)