



Total No. of printed pages = 3

**SUBJECT CODE = ELE022103**

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

**2017**

**End Semester B.Tech. Examination**

**1<sup>st</sup> Semester**

**BASIC ELECTRICAL ENGINEERING**

Full Marks- 70

Pass Marks- 21

Time- 3 hours

---

*The figures in the margin indicate full marks.*

**PART A**

**Q.1. Answer all questions:**

**(16x1=16)**


- Explain short circuit and open circuit.
- Define Linear and non-Linear circuits.
- A 25W, 220V bulb and a 100W, 220V bulb are connected are joined in series with a supply of 220V. Which bulb will glow more brightly?
- You are given three bulbs of 25W, 40W and 60W. Which one will have the lowest resistance?
- Define Form factor and Peak factor.
- Define Average and RMS value of an alternating quantity.
- What are the different standard forms of representing an alternating voltage?
- Draw the circuit diagram and phasor diagram for AC circuit containing pure inductance along with voltage and current equations.
- Define Magnetomotive force and Reluctance.
- Define Self-induced and Mutually-induced emf.
- A magnetic circuit has mmf of 400 AT and a reluctance of  $2 \times 10^5$  AT/Wb. Calculate the magnetic flux.
- In a Star and Delta connected system, what is the relation between the line voltage  $V_L$  and phase voltage  $V_{ph}$  and line current  $I_L$  and phase current  $I_{ph}$ ?
- Write two principles of operation of electrical measuring instruments.
- Name two type of instrument suitable for measuring only d.c instrument.
- What is the difference between Fuse and MCB?
- What is the function of Two-way switches?

## PART B

Q.2. Answer all questions:

(3.5x4=14)

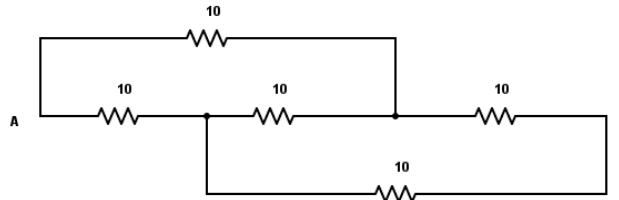- a) Why do we use Star/Delta and Delta/Star Transformation? Calculate the equivalent resistance between the terminals A and B of the following network. The values of resistances are in ohms.




- b) The equation of an alternating current  $i=42.42 \sin 628t$ . Determine (i) its maximum value (ii) frequency (iii) rms value (iv) average value and (v) form factor.
- c) Find the expression for lifting power of a magnet.
- d) Explain the three torques required for an indicating instrument.

## PART C

Q.3. Answer all questions:

(10x4=40)

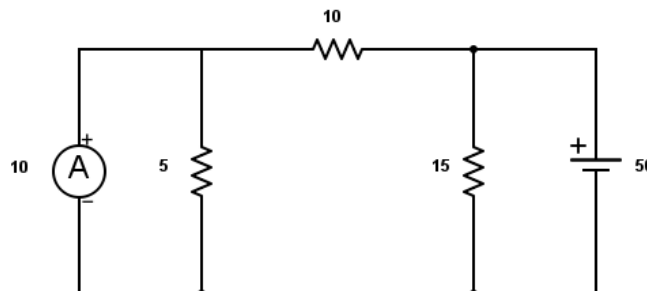
- a) State Thevenin's and Norton's Theorem. Find the current through  $10 \Omega$  resistor as shown in figure below using Thevenin's theorem. The values of resistances, voltage and current are in ohms, volt and amp respectively. 3+5+2



Determine the maximum power that can be transferred to a load resistance connected across  $10 \Omega$ .

OR

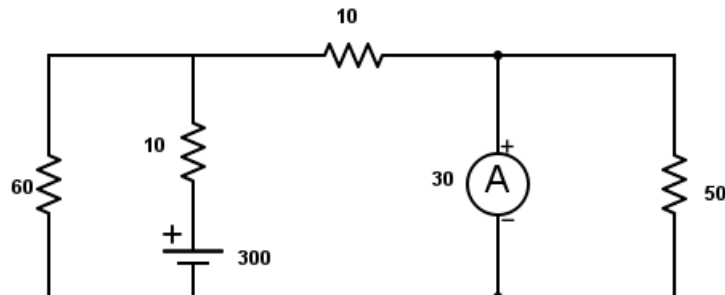State and prove maximum power transfer theorem. Using superposition theorem, find the current through the  $50\Omega$  resistor shown in the figure below. The values of resistances, voltage and current are in ohms, volt and amp respectively. 4+6



- b) Compare the properties of electric and magnetic circuits. A circular iron ring has a mean circumference of  $1.5\text{ m}$  and a cross-sectional area of  $0.01\text{ m}^2$ . A saw-cut of  $4\text{mm}$  wide is made in the iron ring. Calculate the magnetizing current required to produce a flux of  $0.8\text{ mWb}$  in the air gap if the ring is wound with a coil of  $175$  turns. Assume relative permeability of iron as  $400$  and leakage factor  $1.25$ . 4+6

OR

Deduce the expression for Voltages, Currents and Power of a three phase ( $3-\Phi$ ) Star Connected system.

A 3-phase motor load has a p.f. of  $0.397$  lagging. Two wattmeters connected to measure power show the input as  $30\text{kW}$ . Find the reading on each meter. 6+4

- c) Explain briefly the principle of generation of 3-Phase voltages. Give the reasons for the use of 3- phase system. A resistance  $R$ , an inductance  $L=0.01\text{ H}$  and a capacitance  $C$  are connected in series. When an alternating voltage  $v = 400 \sin (3000t - 20^\circ)$  is applied to the series combination, the current flowing is  $10 \sqrt{2} \sin (3000t - 65^\circ)$ . Find the values of  $R$  and  $C$ . 4+6

OR

Deduce the expression for Average and R.M.S. value of Sinusoidal current. What do you mean by phase and phase difference? An iron-cored choke coils has a resistance of  $4\Omega$  when measured by a d.c supply. On a  $240\text{ V}$ ,  $50\text{ Hz}$  mains supply, it dissipates  $500\text{ W}$ , when the current being  $10\text{ A}$ . calculate (i) Impedance (ii) the power factor (ii) the iron loss and (iv) inductance of the coil. 4+2+4

- d) Discuss about five types of accessories required in the domestic electrical installations. Explain briefly, why electrical installations must be earthed. Explain plate earthing in details. 4+2+4

OR

Explain the working of principles of Permanent Magnet moving Coil Instrument and Attraction Type Moving Iron Instrument. Explain the Extension of Ammeter Range. 7+3